 




# Logic Simulation

- Introduction
- Simulation Models
- **Logic Simulation Techniques**
  - ◆ **Compiled-code simulation**
    - \* Logic Optimization
    - \* Logic Levelization
    - \* Code Generation
  - ◆ Event-driven simulation
  - ◆ Parallel Simulation
- Issues of Logic Simulations
- Conclusions


 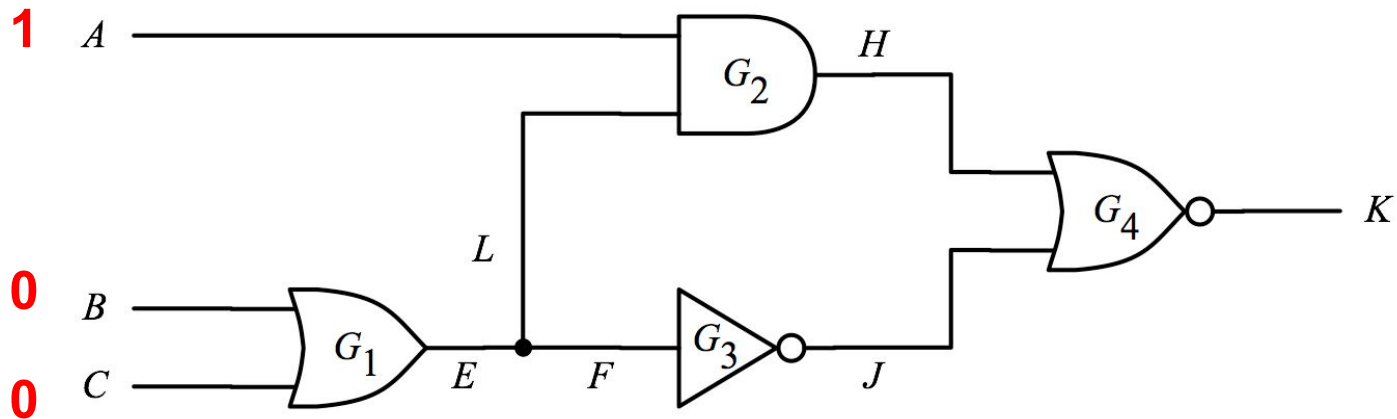
# Compiled-Code Simulation


- Translate circuit into sequence of codes
  - ♦ **Execute codes** = run logic simulation



```
while{true} do
    read(A,B,C);
    E  $\square$  OR(B,C);
    H  AND(A,E);
    J  $\square$  NOT(E);
    K  NOR(H,J);
end
```

$E = \text{OR}(0,0) = 0$   
 $H = \text{AND}(1,0) = 0$   
 $J = \text{NOT}(0) = 1$   
 $K = \text{NOR}(0,1) = 0$



# How to Compile Code?

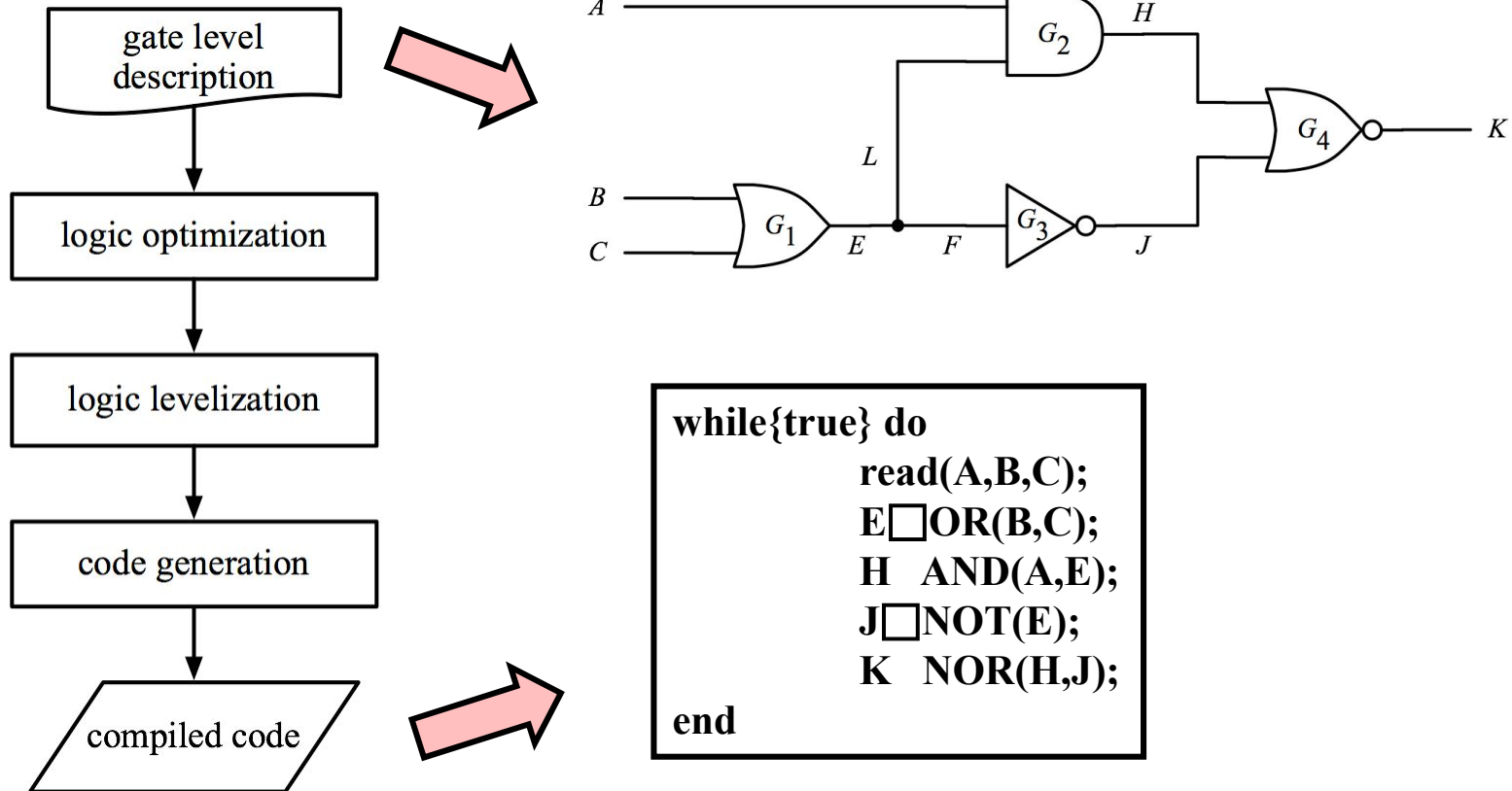

(WWW Fig. 3.12)
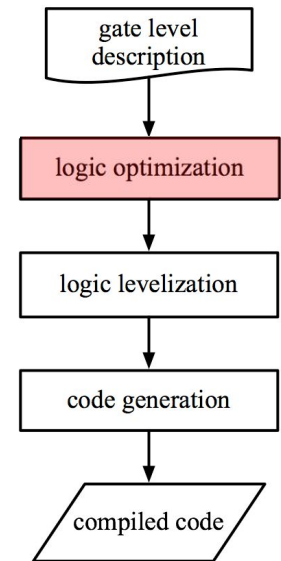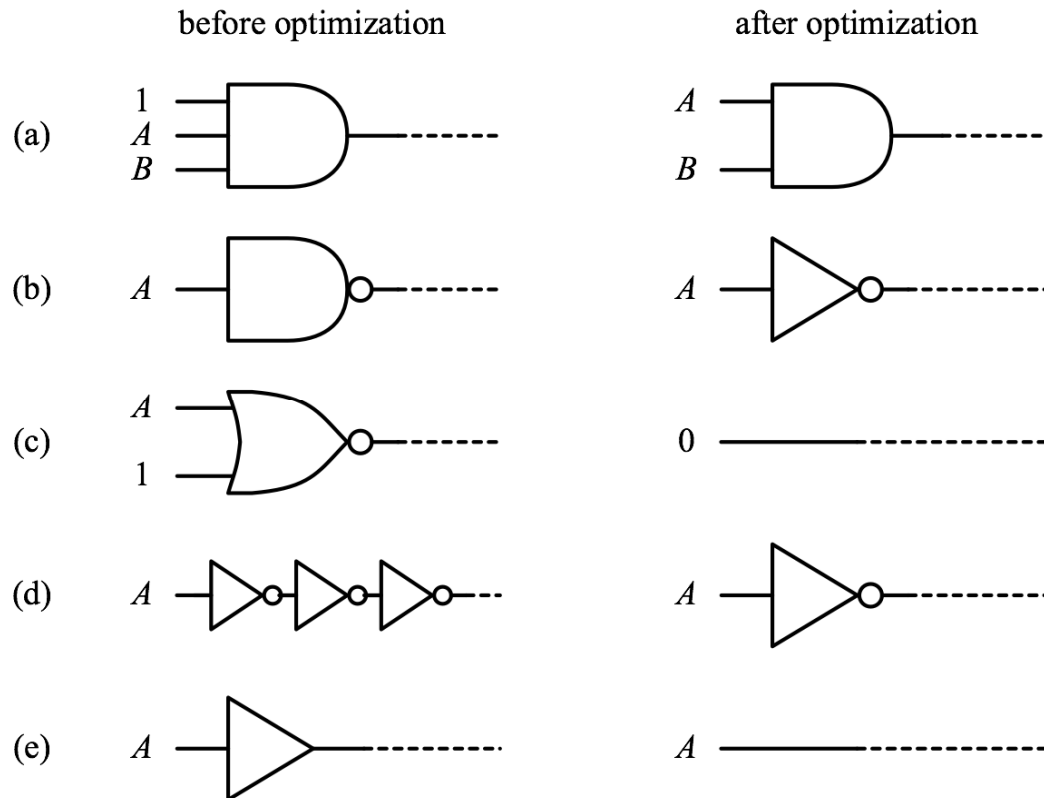
# Logic Optimization


- Simplify logic before generating codes
- Shorten code length and simulation time
- Example (WWW Fig. 3.13)



(b) Code generation flow
 
# Logic Levelization

- **Levelization**: order gate in sequence such that
  - ♦ a gate won't be evaluated until
  - ♦ all its driving gates have been evaluated




**correct**

```
while{true} do
  read(A,B,C);
  E ← OR(B,C);
  H ← AND(A,E);
  J ← NOT(E);
  K ← NOR(H,J);
end
```


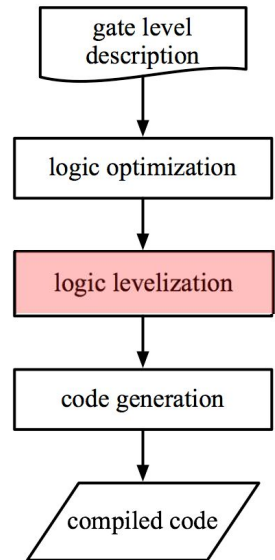
**wrong**

```
while{true} do
  read(A,B,C);
  H ← AND(A,E);
  E ← OR(B,C);
  J ← NOT(E);
  K ← NOR(H,J);
end
```



(b) Code generation flow

**Levelization Ensures Correct Order**

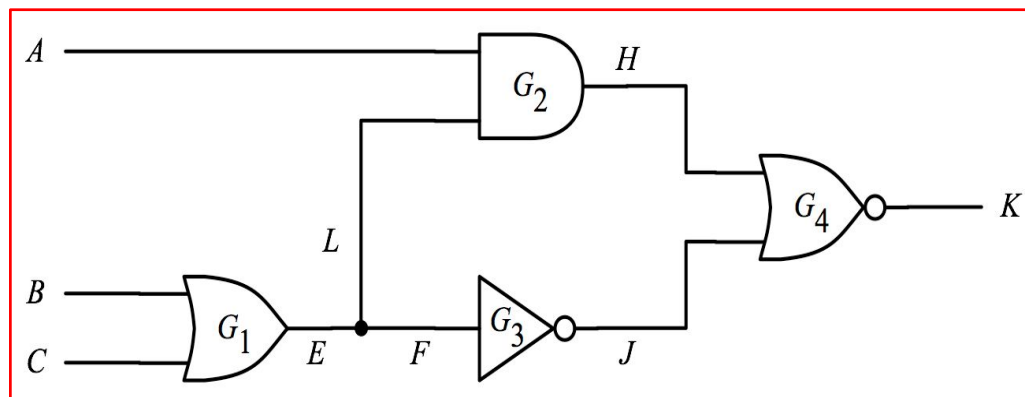 

(WWW Fig 3.17)

$g$  = gate

$l$  = level



$Q$  = queue (FIFO)

step	A	B	C	$G_1$	$G_2$	$G_3$	$G_4$	$Q$ <front, back>
0	0	0	0					< $G_2$ , $G_1$ >
1	0	0	0					< $G_1$ , $G_2$ > put $G_2$ back
2	0	0	0	1				< $G_2$ , $G_2$ , $G_3$ >
3	0	0	0	1	2			< $G_2$ , $G_3$ , $G_4$ >
4	0	0	0	1	2			< $G_3$ , $G_4$ , $G_4$ > why? FFT
5	0	0	0	1	2	2		< $G_4$ , $G_4$ , $G_4$ >
6, 7, 8	0	0	0	1	2	2	3	< >

# Quiz

Q: Please levelize this circuit

A:

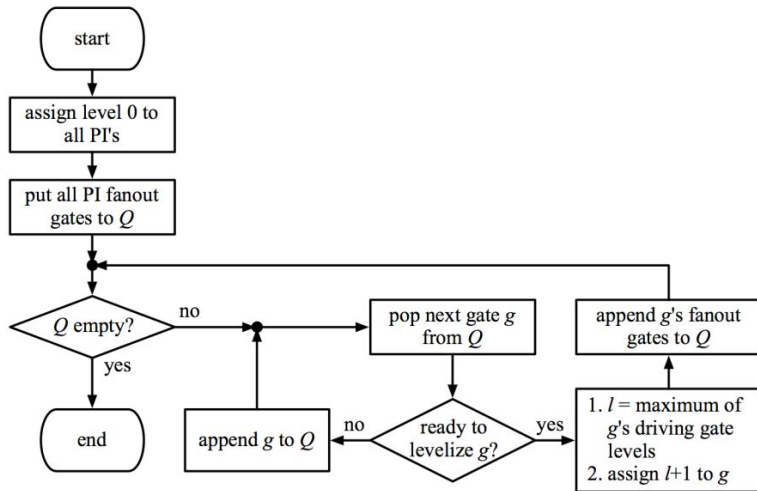 

step	A	B	C	$G_1$	$G_2$	$G_3$	$G_4$	$Q$ <front, back>
0	0	0	0					< $G_1, G_2, G_3$ >
1								
2								
3								
4								
5								
6								

# Code Generation

## ① High-level code (like C)

😊 Portable, easy debug

😞 Need compilation every time circuit changed

## ② Machine code

😊 Fast to run


😞 Not portable, hard to debug

## ③ Interpreted code


(at run time, codes are interpreted and executed)

😊 Portable, easy debug

😞 Slower than machine code

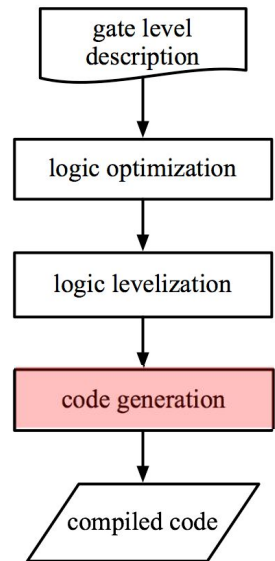

(b) Code generation flow

 

```
while{true} do
    read(A,B,C);
    E ← OR(B,C);
    H ← AND(A,E);
    J ← NOT(E);
    K ← NOR(H,J);
end
```



# Summary

- **Compiled-code simulation:** convert gates into **codes** for evaluation
  - ◆ **Optimization:** simplifies logic
  - ◆ **Levelization:** sort gates in order (*i.e.* topological sort of graph)
  - ◆ **Code generated:** 1.high-level, 2.machine, 3.interpreted



## 😊 Pros

- ◆ **Simple** to implement
- ◆ Can speed-up by **parallelism**
  - \* see parallel simulation

## 😞 Cons

- ◆ Only ***cycle-based accuracy***, no timing (zero gate delay)
- ◆ Need to evaluate **whole circuit** even only small portion changed
  - \* see event-driven simulation

# FFT

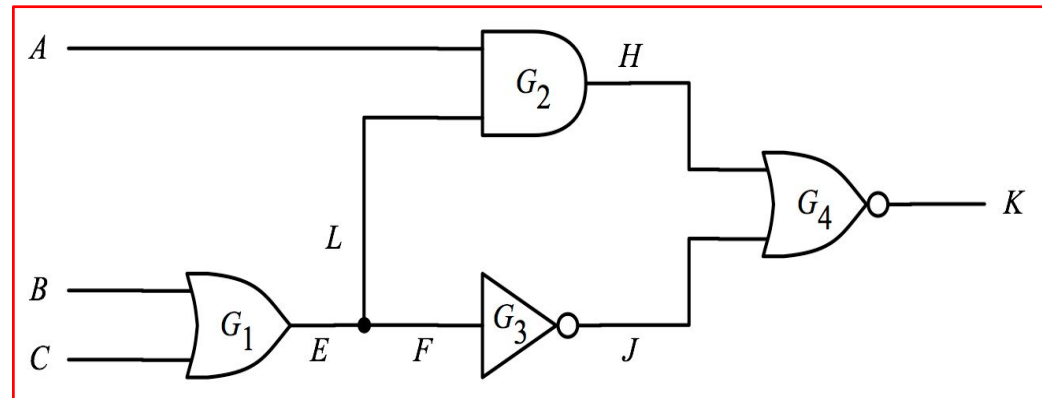 

(WWW Fig 3.17)

$g$  = gate


$l$  = level

$Q$  = queue (FIFO)

step	A	B	C	$G_1$	$G_2$	$G_3$	$G_4$	$Q$ <front, back>
0	0	0	0					< $G_2$ , $G_1$ >
1	0	0	0					< $G_1$ , $G_2$ >
2	0	0	0	1				< $G_2$ , $G_2$ , $G_3$ > why $G_2$ again?
3	0	0	0	1	2			< $G_2$ , $G_3$ , $G_4$ >
4	0	0	0	1	2			< $G_3$ , $G_4$ , $G_4$ > why $G_4$ again?
5	0	0	0	1	2	2		< $G_4$ , $G_4$ , $G_4$ >
6, 7, 8	0	0	0	1	2	2	3	<>

 
# FFT

- Q:How to levelize SR latch?
  - ♦ with feedback





 
# Appendix: Logic Symbols

- IEEE logic symbols: rectangular shape v.s. distinctive shape
- AND



- Or

   

- inverter

