 



Fault Modeling

- Introduction
- **Fault Models**
 - ◆ Stuck-at fault (1961)
 - ◆ Bridging fault (1973)
 - ◆ Delay fault (1974)
 - ◆ Transistor-level fault
 - * Stuck-open (1978)
 - * Stuck-on
 - * Cell-aware (2009)
 - ◆ Review
- Fault Detection
- Fault Coverage
- Conclusion



Why Faulty NAND Has Memory ?

- Stanford Murphy Experiment [Li 01]
 - ♦ **Sequence Dependency**: Test result depends on test sequence
- Example: NAND gate
 - ♦ Same test patterns {11, 01, 00}, but in different sequence
 - ♦ Sequence 1 **fails**; Sequence 2 **passes**
 - ♦ Is it **A SA1** or not?

 

Sequence 1

A	B	Out _{good}	Out _{faulty}
1	1	0	0
0	1	1	0
0	0	1	1

← A SA1 ?


Sequence 2

A	B	Out _{good}	Out _{faulty}
0	0	1	1
0	1	1	1
1	1	0	0

← Not A SA1 ??


**SSF Cannot
Explain Seq. Dep.**

Classification of Fault Models

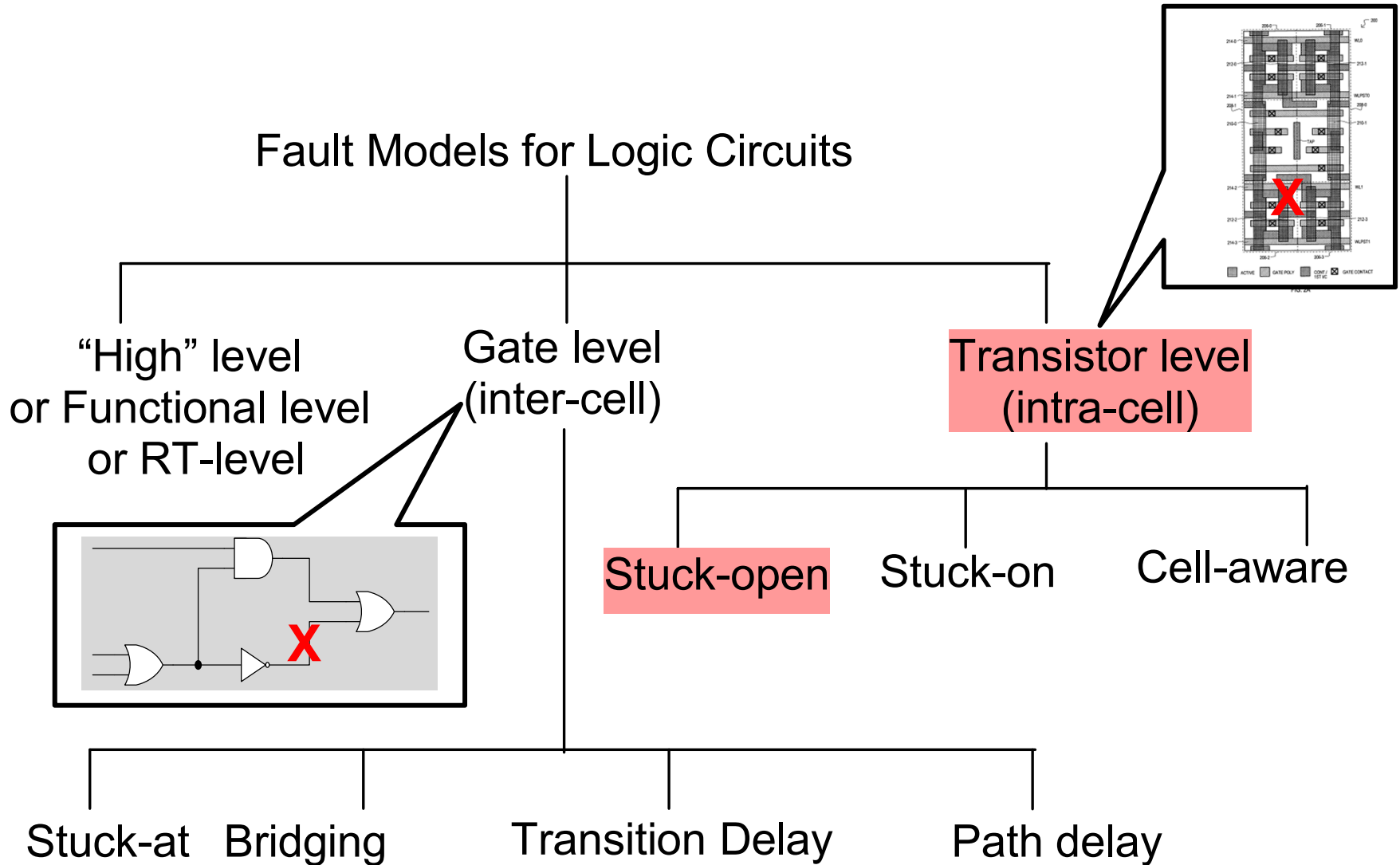

Stuck-open Fault [Wadsack 78]

 - **Stuck-open (SOP) fault**
 - ♦ Faulty transistors is always off
- **Example: NAND**
 - ♦ **11→01** detects A_P SOP
 - ♦ **Totally 4 faults: $A_P B_P A_N B_N$**




Input A B	Fault-free Output	Faulty Outputs Z = high impedance			
		A_P	A_N	B_P	B_N
0 0	1	1	1	1	1
0 1	1	Z	1	1	1
1 0	1	1	1	Z	1
1 1	0	0	Z	0	Z

SOP Requires 2-pattern Test

Sequence Dependency

- SOP Faulty circuit has *memory* (due to parasitic capacitor)
 - ♦ Test results *depend on sequence of test patterns*
- Example: A_p stuck-open fault,
 - ♦ Same test patterns {11, 01, 00}, but different sequence
 - ♦ Sequence 1 **fails**; Sequence 2 **passes** (test escape)

 

Sequence 1

A	B	Out _{good}	Out _{faulty}
1	1	0	0
0	1	1	0
0	0	1	1

FAIL:
Fault detected

Sequence 2

A	B	Out _{good}	Out _{faulty}
0	0	1	1
0	1	1	1
1	1	0	0

PASS:
Fault undetected
(test escape)

Simulation Results [Millman 89]


- Q: How effective is SSF test sets for stuck-open faults?
- 74LS181 ALU
 - ◆ Total **426** stuck-open faults
 - ◆ 100% SSF tests cannot achieve 100% SOP fault coverage

Test set	Krish	Br2	Goel	Mc1	Hugh
Test Length	12	14	35	124	135
SSF fault coverage %	100	100	100	100	100
SOP fault coverage %	79.3	79.6	90.8	87.1	93.4

SSF Not Enough for SOP

SOP \neq TDF [Li 02]

 - TDF is correlated with SOP fault, but they are **NOT** the same
- $\{11 \rightarrow 01, 01 \rightarrow 10, 00 \rightarrow 11\}$ has **100%** TDF coverage
 - ♦ but only **75%** SOP fault coverage (missed B_p)



$A_1 B_1 \rightarrow A_2 B_2$	Out_{good}	Detected SOP	Detected TDF
11 \rightarrow 01	0 \rightarrow 1	A_p	A STF; Out STR
10 \rightarrow 01	1 \rightarrow 1	-	A STF
11 \rightarrow 10	0 \rightarrow 1	B_p	B STF; Out STR
01 \rightarrow 10	1 \rightarrow 1	-	B STF
00 \rightarrow 11	1 \rightarrow 0	$A_N B_N$	A STR; B STR Out STF

TDF Not Enough for SOP, Either

Experimental Results [Woodhal 87] [Li 01]

- 1 μm CMOS [Woodhal 87]
 - ◆ Total population: 4,552 chips (passed parametric test)
 - * 1,225 chips failed stuck-at test
 - * 44 chips (3.6% of 1225) failed stuck-open test
 - * 4 chips failed stuck-open test **escaped** stuck-at test
- 0.7 μm CMOS, *Stanford Murphy experiment* [Li 01]
 - ◆ Total population 5.5K chips tested
 - * 116 defective chips
 - * 7 single stuck-open fault diagnosed
 - * 2 multiple faults (stuck-at + stuck-open)
- About 5% of failed chips are stuck-open

Stuck-open Cannot be Ignored


Quiz

Q1: Find a sequence of 2 patterns to detect B_N SOP fault in NOR

A:

Q2: Find a sequence of 2 patterns that cannot detect B_N SOP fault (test escape)

A:

 


Sequence 1

A	B	Out _{good}	Out _{faulty}

Sequence 2


A	B	Out _{good}	Out _{faulty}

Classification of Fault Models

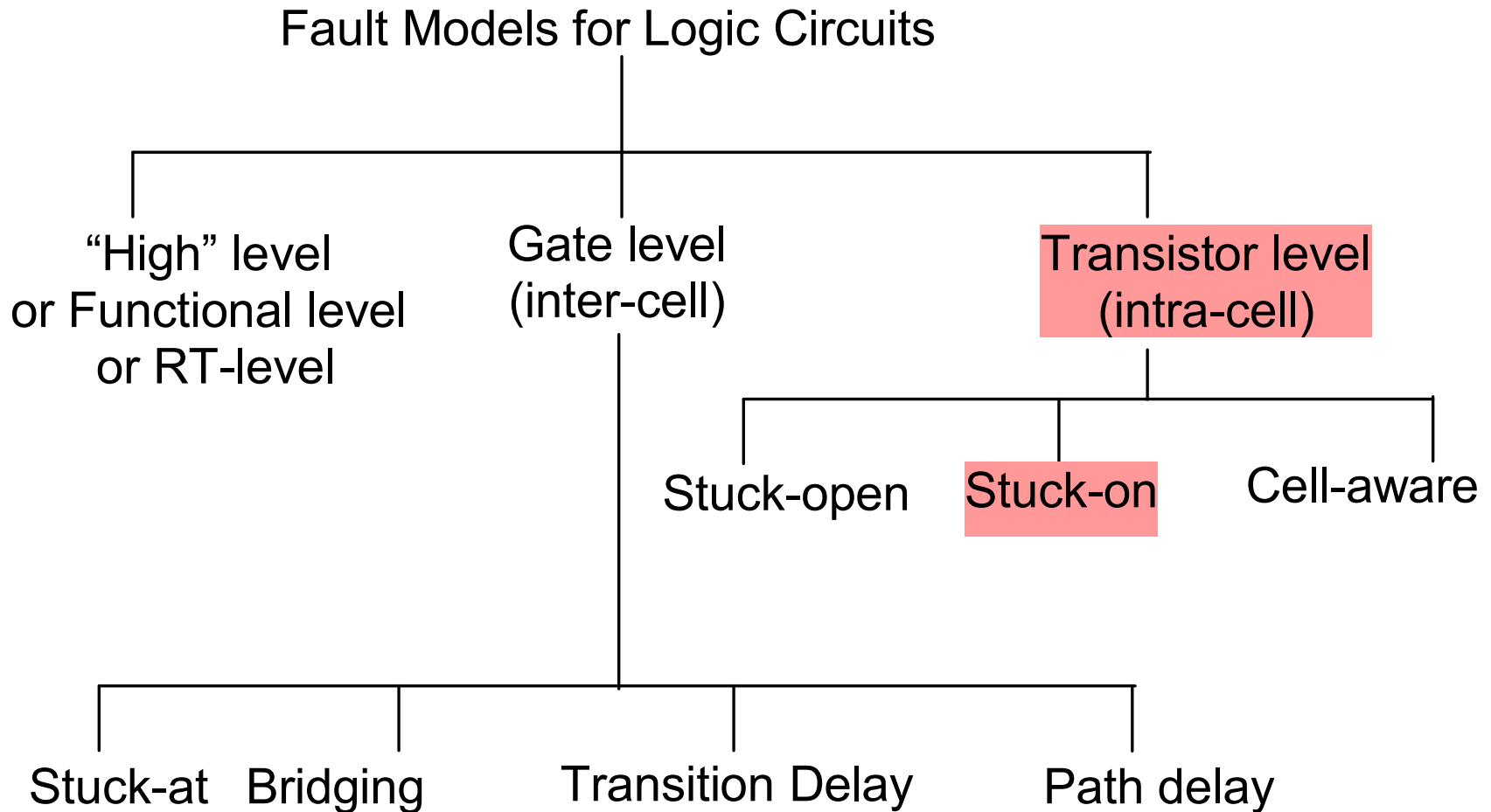

Stuck-On Fault


 
- Faulty transistor is always on
 - ♦ Form a conducting path between Vdd and Gnd in static state
- Stuck-on fault may NOT be detected by Boolean testing
 - ♦ Output logic values depends on relative impedance of transistors
- Stuck-on fault can be detected by I_{DDQ} testing
 - ♦ Apply test pattern
 - ♦ Wait for a while
 - ♦ Measure *quiescent current* from power supply



I_{DDQ} Testing [Mark 81]

- Measure static power supply current, with test patterns applied
 - ♦ I_{DD} = power supply current from V_{DD}
 - ♦ Q = quiescent
- Very commonly used in CMOS technology*
- Example: NMOS stuck-on fault

  
*but I_{DDQ} less effective for new technologies due to leakage




Quiz

Q: Find a test pattern to detect B_N Stuck-on fault in NOR by I_{DDQ}

A:


 


Classification of Fault Models

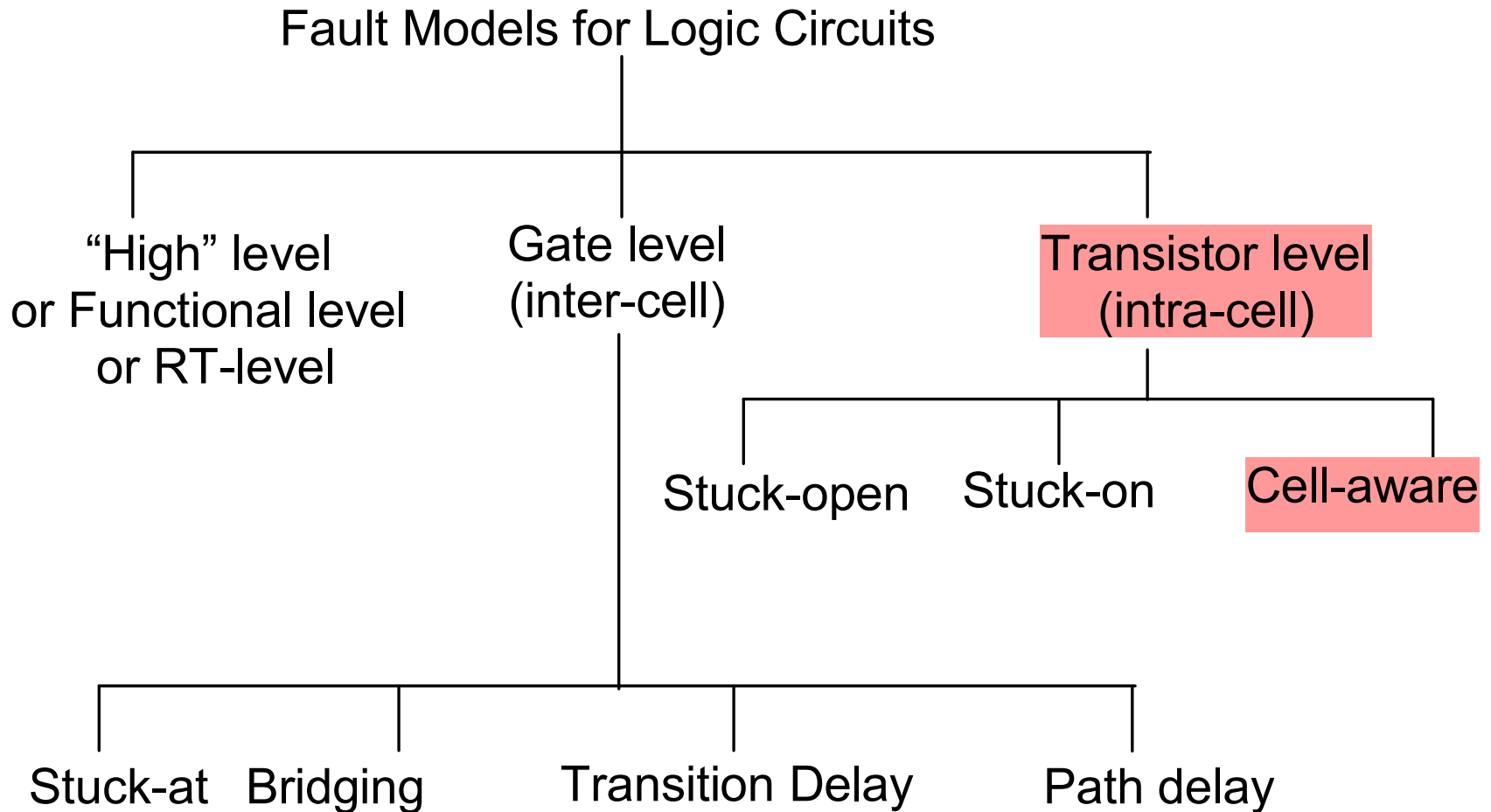


Cell-aware Test (CAT) [Hapke 09]

  - Consider different defects types inside cell: **open, bridge, transistor**
- Need *layout extraction* and *analog fault simulation*




PFA proven CAT only detected defect

 

Why CAT more Effective?


- 4 test patterns detect 8 SSF at MUX I/O pins
 - ◆ 100% SSF coverage

in_0	in_1	ctrl	out	detected SSF
0	1	0	0	ctrl SA1, out SA1, in_0 SA1
1	0	0	1	in_1 SA1
1	0	1	0	ctrl SA0, out SA0, in_0 SA0
1	1	1	1	in_1 SA0

 

- CAT adds {000} to detect in_1/w bridging


in_0	in_1	ctrl	out
0	1	0	0
1	0	0	1
1	0	1	0
1	1	1	1
0	0	0	0/1

 

**CAT is Effective
but Longer**

Experimental Results [Hapke 14]

 
- AMD 32 nm, total **800K** IC tested
- **699** IC failed only CAT, passed other tests




CAT Improves 885DPM

Fault Modeling

 - Introduction
- **Fault Models**
 - ◆ Stuck-at fault (1961)
 - ◆ Bridging fault (1973)
 - ◆ Delay fault (1974)
 - ◆ Transistor-level fault (1978)
 - ◆ **Review**
- Fault Detection
- Fault Coverage
- Conclusion



Classification of Fault Models

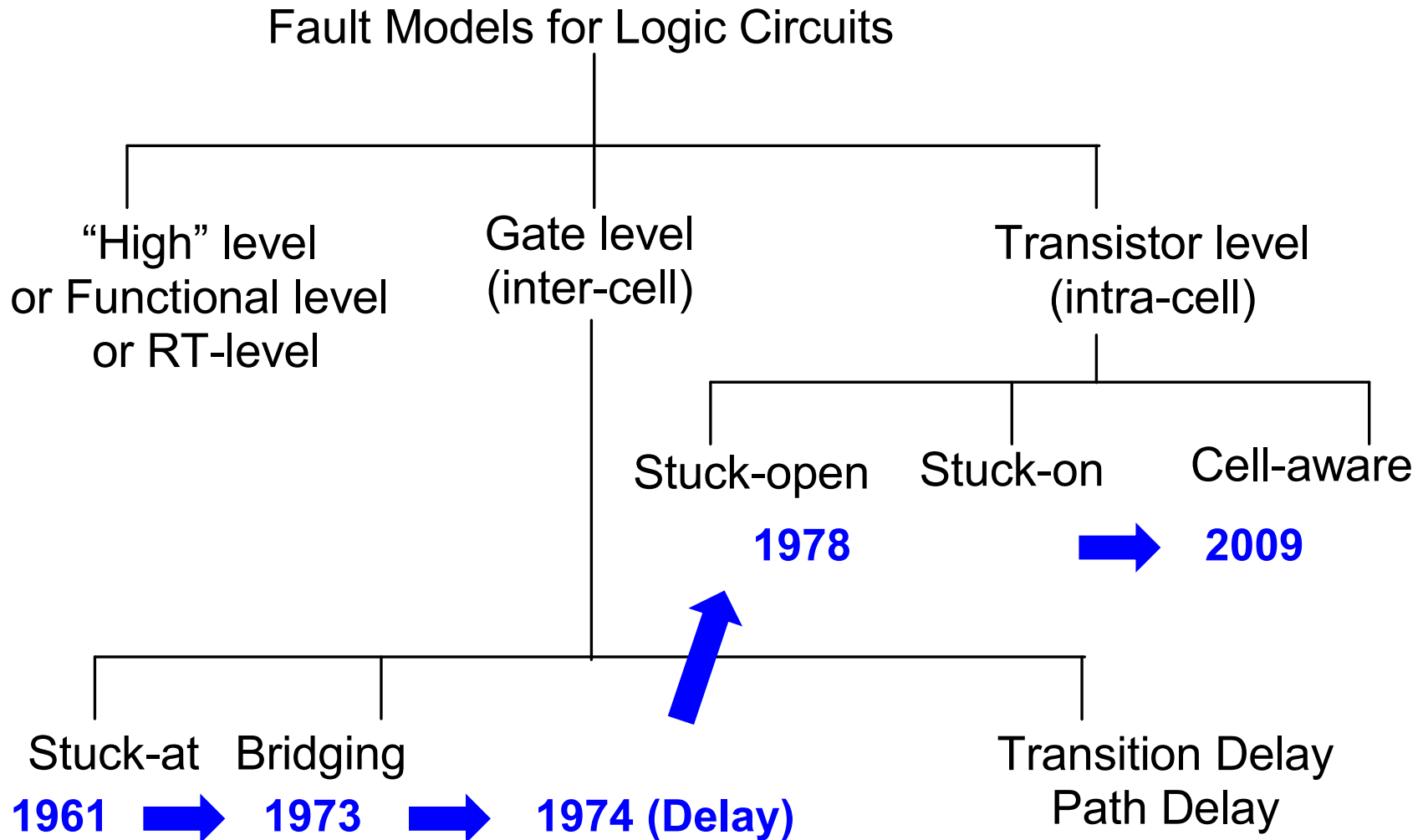

Fault Models Evolve with Technology

More Classifications

- According to timing
 - ♦ **AC faults**: timing dependent
 - * Delay faults
 - ♦ **DC faults**: not timing dependent
 - * Stuck-at faults, stuck-open faults ...
- According to memory effect
 - ♦ **Sequential faults**: faults that increase number of states
 - * Stuck-open faults, feedback bridging faults
 - ♦ **Combinational faults**: faults do not increase number of states
 - * Stuck-at faults, non-feedback bridging faults
- According to circuit under test (CUT)
 - ♦ **Memory** fault model (see *memory testing* chapter)
 - ♦ **FPGA** fault model
 - ♦ ...

No Single Best Fault Model for All Circuits

Summary

① Transistor stuck-open (SOP)

- ♦ **Sequence dependence: faulty comb. logic has memory**
- ♦ **TDF \neq SOP**

② Transistor stuck-on

- ## ♦ I_{DDQ} testing

③ Cell-aware testing

- ◆ layout extraction + analog fault simulation
- ◆ Improved DPM but longer test

- **Fault models evolve with technology**

- ◆ **NO single best fault model** for all circuits
- ◆ **New fault models needed for future technologies!**

